

1. Design a programmable circuit block with the following specifications. Show your implementation.
- a. Input ports: A, B
 - b. Clock input port: clk
 - c. Output port: Q
 - d. Configuration inputs: C1, C2
 - e. Its functions are given below:

C1 C2	Circuit function
0 0	Positive edge triggered DFF, the DFF input is A and output is Q
0 1	Negative edge triggered DFF, the DFF input is B and output is Q
1 0	Positive edge triggered DFF, the DFF input is (A+B) and output is Q
1 1	Circuit output is at high impedance state


SYSTEM BOM

① 2-TO-1 MUX FOR f & z CLK


② OR GATE

③ MUX TO SELECT SIGNAL THROUGH OR GATE.

④ TRI-STATE BUFFER

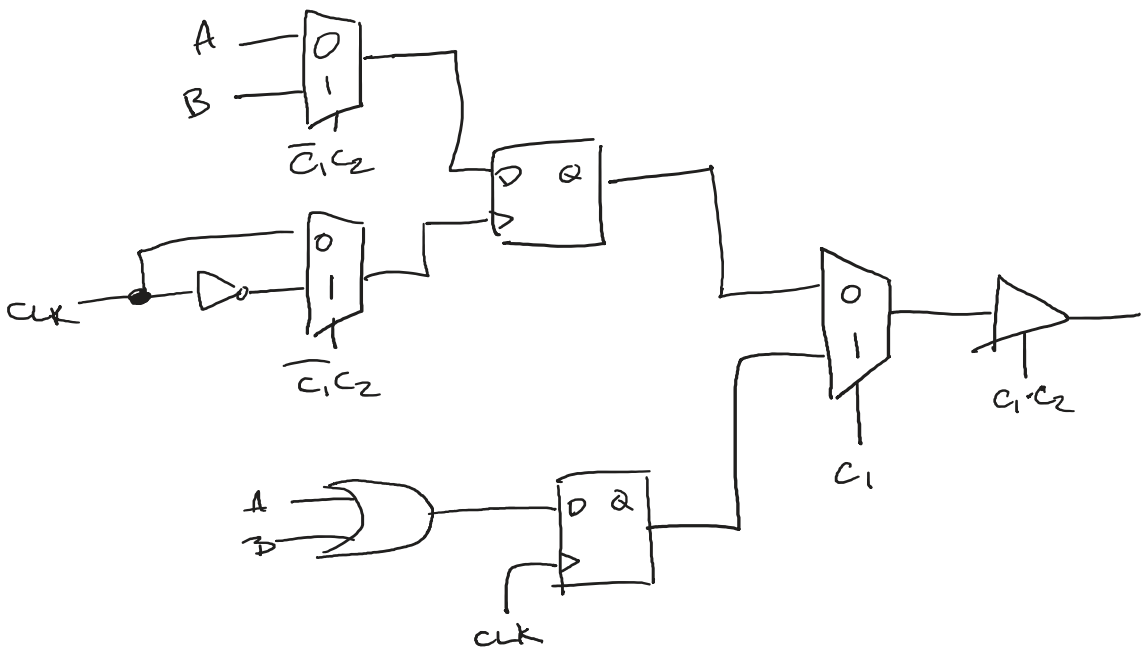

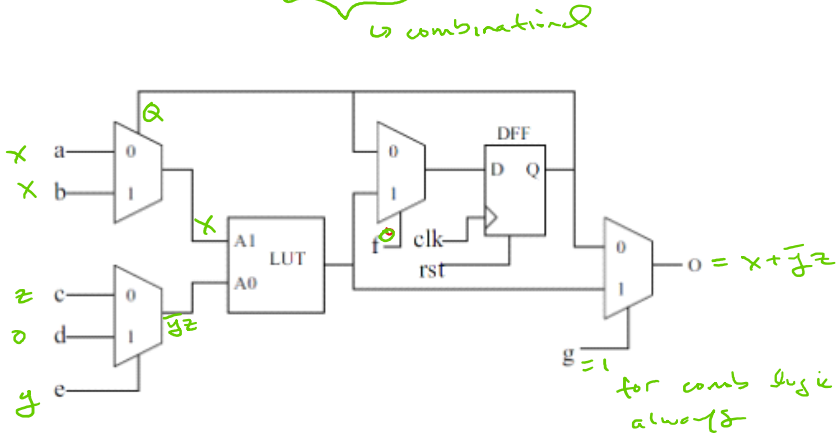2. The following is a programmable cell. Fill the following tables to show how to program the cell for implementing function $O = x + \bar{y} \cdot z$



a	b	c	d	e	f	g
x	x	z	0	y	0	1

(Fill the tabel with 0, 1, x, y, z)

Address A1 A0	00	01	10	11
$\{x, \bar{y}z\}$	0	1	1	1

